

# Tutorial 1, Sep 15, 2025

- 3 approaches to control:
  - State space – pioneered by Kalman
  - Transfer function – classical approach
  - Behavioural – data-driven approach (instead of explicit modelling)
- Consider a standard RLC circuit
  - From KVL:  $u - Ri - L \frac{di}{dt} - v = 0$
  - From KCL:  $i = C \frac{dv}{dt}$
  - Input  $u$  is the voltage across a voltage source
  - Method 1:  $0 = u - RC \frac{dv}{dt} - L \frac{d}{dt} \left( C \frac{dv}{dt} \right) - v$ 
    - \*  $-LC \frac{d^2v}{dt^2} - RC \frac{dv}{dt} - v + u = 0$
    - \* This is the *input-output* form of the system
    - \* Let  $\mathbf{x} = \begin{bmatrix} v \\ \frac{dv}{dt} \end{bmatrix}$
    - \*  $\dot{\mathbf{x}} = \begin{bmatrix} \frac{dv}{dt} \\ \frac{d^2v}{dt^2} \end{bmatrix} = \begin{bmatrix} \frac{dv}{dt} \\ \frac{1}{LC}(-RC \frac{dv}{dt} - v + u) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \mathbf{x} + \begin{bmatrix} 0 \\ \frac{1}{LC} \end{bmatrix} u = \mathbf{A}\mathbf{x} + \mathbf{B}u$
    - \* Now we construct the output equation since we cannot directly measure all components of  $\mathbf{x}$
    - \*  $y = v = [1 \ 0] \mathbf{x} + 0u = \mathbf{C}\mathbf{x} + \mathbf{D}u$
  - Method 2:  $\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -L \frac{di}{dt} - Ri - v + u \\ -C \frac{di}{dt} + i \end{bmatrix}$ 
    - \*  $0 = \begin{bmatrix} -L & 0 \\ 0 & -C \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i \\ v \end{bmatrix} + \begin{bmatrix} -R & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i \\ v \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u$
    - \* This is similar to the input-output form we had before, but in a vector form
  - Generally the number of state variables we need is the number of derivatives times the number of variables
    - \* In the first method we used a second derivative, and only  $v$  as output
    - \* In the second method we used only first order derivatives but both  $v$  and  $i$  as output